

# Experiment 3 – Function Generator

Mehdi  
Jamalkhah,  
810100111

Mobina  
Mehrazar,  
810100216

**Abstract**— This document is a report for experiment #3 of Digital Logic Design Laboratory at ECE department, University of Tehran. The purpose of this experiment is to generate a wide variety of waveforms with different amplitude and frequency with an Arbitrary Function Generator (AFG).

**Keywords**— Sine, reciprocal, frequency, FPGA, DDS, waveform, clock, module, Verilog, ROM.

## I. INTRODUCTION

The goal of this report is to design an Arbitrary Generator that is capable of generating reciprocal, square, triangle, sine, full-wave rectified, and half-wave rectified.

 


Fig. 1 Block diagram of the Arbitrary Generator (AFG) : there is a main component that generates one of the desired waveform based on the function selectors' value, a frequency selector that sets the output signal frequency, and amplitude selector. DAC is also used to convert the digital output to an analog signal, which can be observed and evaluated via an oscilloscope. A ROM memory is usually embedded to store any other arbitrary waveform.

## II. WAVEFORM GENERATOR

This part of project produces desired functions. Output of this module is an 8-bit digital representing the amplitude of signal.

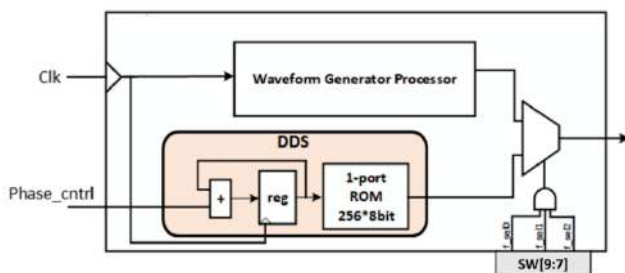


Fig. 2 Block diagram of waveform generator

Waveforms square, reciprocal and triangle are based on a counter that counts up or down with each clock for the period of the waveform.

### A. Reciprocal

This waveform will be created by following formula:

$$Rep(x) = \frac{255}{(255 - x) + 1}$$

Where x is the output of counter.

```
1 timescale 1ns/1ns
2
3 module ReciprocalWave(clk, rst, ReciprocalWave);
4 input clk, rst;
5 output reg [7:0] ReciprocalWave = 8'd0;
6
7 reg [7:0] count_out = 8'b0;
8
9 always @(posedge clk) begin
10
11     if (rst) begin
12         ReciprocalWave = 8'b0;
13     end
14
15     else if (count_out == 8'b0) begin
16         ReciprocalWave = 8'b0;
17     end
18
19     else begin
20         ReciprocalWave = 8'd255 / (8'd255 - count_out + 8'd1);
21     end
22 end
23
24
25 always @(posedge clk) begin
26
27     if (rst) begin
28         count_out = 8'b0;
29     end
30
31     else begin
32         count_out = count_out + 1;
33     end
34 end
35
36 endmodule
37
```

Fig. 3 Reciprocal Verilog code

### B. Square

```

1 | `timescale 1ns/1ns
2 |
3 | module SquareWave(clk, rst, squareWave);
4 |   input clk, rst;
5 |   output reg [7:0] squareWave = 8'b1111_1111;
6 |
7 |   reg [7:0] count_out = 8'b0;
8 |
9 |   always @(posedge clk) begin
10 |
11 |       if (rst) begin
12 |           squareWave = 8'b1111_1111;
13 |       end
14 |
15 |       else if (count_out > 8'd128 == 8'd0) begin
16 |           squareWave = ~squareWave;
17 |       end
18 |
19 |   end
20 |
21 |   always @(posedge clk) begin
22 |
23 |       if (rst) begin
24 |           count_out = 8'b0;
25 |       end
26 |
27 |       else begin
28 |           count_out = count_out + 1;
29 |       end
30 |
31 |   end
32 | endmodule

```

Fig. 3 Square Verilog code

### C. Triangle

This wave can be created by following formula:

$$Triangle(x) = x$$

Where x is output of counter.

```

1 | `timescale 1ns/1ns
2 |
3 | module TriangleWave(clk, rst, TriangleWave);
4 |   input clk, rst;
5 |   output reg [7:0] TriangleWave = 8'd0;
6 |
7 |   reg [7:0] count_out = 8'b0;
8 |
9 |   always @(posedge clk) begin
10 |
11 |       if (rst) begin
12 |           TriangleWave = 8'd0;
13 |       end
14 |
15 |       else if (count_out > 8'd128) begin
16 |           TriangleWave = 8'd128 - (count_out - 8'd128);
17 |       end
18 |
19 |       else begin
20 |           TriangleWave = count_out;
21 |       end
22 |
23 |   end
24 |
25 |   always @(posedge clk) begin
26 |
27 |       if (rst) begin
28 |           count_out = 8'b0;
29 |       end
30 |
31 |       else begin
32 |           count_out = count_out + 1;
33 |       end
34 |
35 |   end
36 | endmodule

```

Fig. 4 Triangle Verilog code

### D. Sine types

The full-wave and half-wave rectified waveforms are both generated based on the sine wave. The following second order differential equation can be used to generate the sine function:

$$\sin(n) = \sin(n - 1) + a \times \cos(n - 1)$$

$$\cos(n) = \cos(n - 1) - a \times \sin(n)$$

In order to do the mathematical operations with reasonable accuracy, operations are done in 16-bit fixed point. Also, considering the period of about 256 clock cycles from frequency selector, the equations turn to:

$$\sin(n) = \sin(n - 1) + \frac{1}{64} \times \cos(n - 1)$$

$$\cos(n) = \cos(n - 1) - \frac{1}{64} \times \sin(n)$$

0 was used for sin(0) and 30000 was used for cos(0). The values are between -32768 to 32767 for sin and cos.

```

3 | `define SIN_0 16'd0
4 | `define COS_0 16'd30000
5 | `define OFFSET 8'd127
6 |
7 | module SineAndRectifiedWave(clk, rst, sinWave, fullRectifiedWave, halfRectifiedWave);
8 |   input clk, rst;
9 |   output reg [7:0] sinWave = `SIN_0;
10 |   output reg [7:0] fullRectifiedWave = `SIN_0;
11 |   output reg [7:0] halfRectifiedWave = `SIN_0;
12 |
13 |   reg [15:0] sin_out = `SIN_0, cos_out = `COS_0, fullRectified = `SIN_0, halfRectified = `SIN_0;
14 |   reg [7:0] sin_out_offset, cos_out_offset;
15 |   reg [7:0] count_out = 8'b0;
16 |
17 |   always @(posedge clk) begin
18 |       if (rst) begin
19 |           sin_out = `SIN_0;
20 |           cos_out = `COS_0;
21 |           fullRectified = `SIN_0;
22 |           halfRectified = `SIN_0;
23 |       end
24 |
25 |       else begin
26 |           sin_out = sin_out + ((cos_out[15:8]), cos_out[15:8]);
27 |           cos_out = cos_out - ((sin_out[15:8]), sin_out[15:8]);
28 |           fullRectified = (sin_out[15]) ? ~sin_out : sin_out;
29 |           halfRectified = (sin_out[15]) ? 16'b0 : sin_out;
30 |
31 |           sin_out_offset = sin_out[15:8] + `OFFSET;
32 |           cos_out_offset = cos_out[15:8] + `OFFSET;
33 |           sinWave = sin_out_offset;
34 |           fullRectifiedWave = fullRectified[15:8];
35 |           halfRectifiedWave = halfRectified[15:8];
36 |       end
37 |
38 |   always @(posedge clk) begin
39 |       if (rst) begin
40 |           count_out = 8'b0;
41 |       end
42 |
43 |       else begin
44 |           count_out = count_out + 1;
45 |       end
46 |
47 |   end
48 | endmodule

```

Fig. 5 Sine, full-rectified, and half-rectified Verilog code

The top level of this part can be seen in following picture.

```

1 | `define SIN_0 16'd0
2 | `define COS_0 16'd30000
3 | `define OFFSET 8'd127
4 |
5 | `timescale 1ns/1ns
6 | module WaveformGenerator(clk, rst, waveSelector, dataOut, romIn);
7 |   input clk, rst;
8 |   input [2:0] waveSelector;
9 |   input [7:0] romIn;
10 |   output reg [7:0] dataOut;
11 |
12 |   wire [7:0] reciprocalWave, squareWave, triangleWave, sinWave, fullRectifiedWave, halfRectifiedWave;
13 |
14 |   ReciprocalWave Reciprocal(.clk(clk), .rst(rst), .ReciprocalWave(reciprocalWave));
15 |   SquareWave Square(.clk(clk), .rst(rst), .squareWave(squareWave));
16 |   TriangleWave Triangle(.clk(clk), .rst(rst), .triangleWave(triangleWave));
17 |   SineAndRectifiedWave Sine(.clk(clk), .rst(rst), .sinWave(sinWave), .fullRectifiedWave(fullRectifiedWave), .halfRectifiedWave(halfRectifiedWave));
18 |
19 |   always @(waveSelector, reciprocalWave, squareWave, triangleWave, sinWave, fullRectifiedWave, halfRectifiedWave) begin
20 |       dataOut = 8'b0;
21 |
22 |       case (waveSelector)
23 |           3'b000: dataOut = reciprocalWave;
24 |           3'b001: dataOut = squareWave;
25 |           3'b010: dataOut = triangleWave;
26 |           3'b011: dataOut = sinWave;
27 |           3'b100: dataOut = fullRectifiedWave;
28 |           3'b101: dataOut = halfRectifiedWave;
29 |           3'b110: dataOut = romIn;
30 |           default: dataOut = 8'b0;
31 |       end
32 |   end
33 | endmodule

```

Fig. 6 waveform generator Verilog code

The results of the sine and cosine operations are signed and range between -127 to +128. However, for simplification and compatibility with other parts of this experiment, an offset of 127 was added to make the range of our signal between 0 and 256.

Most modern function generators use Direct Digital Synthesis (DDS) to produce their output waveforms. DDS generates a tunable output with arbitrary phase from a fixed-frequency reference clock, such as an oscillator. The output of the DDS module is a quantized version of the output waveform, typically a sinusoid, controlled by a phase control value. To generate the DDS signal, a 1-port ROM memory is used to store the values of a sine wave for several clock cycles, which are initialized using a file named sine.mif. An address location is generated using a register and adder, which increments the phase of the signal by the value of the Phase\_cntrl. This module is commonly known as a phase accumulator. The DDS module requires a stable clock frequency, which in this case is a 50-MHz clock frequency of the FPGA. However, the clock frequency will be changed to the ring oscillator divided clock in the subsequent sections of the design.

```

1  `timescale 1ns/1ns
2
3  module DDS(clk, rst, romSinWave);
4      input clk, rst;
5      output romSinWave;
6      reg [7:0] counter = 8'b0;
7      always @(posedge clk) begin
8          if (rst) begin
9              counter = 8'b0;
10         end
11         else begin
12             counter = counter + 1;
13         end
14     end
15     assign romSinWave = counter;
16 endmodule
17

```

Fig. 7 DDS Verilog code (without memory part)

We are going to use different method to implement memory for DDS module.

In first attempt we simply use the ROM megafunction, lpmrom, in the Quartus Megawizard Plug-In.

We can also write Verilog description of memory. By default the Quartus put our memory in logic elements(Fig. 11), but this part of FPGA is so important in some designs. So we have this option to forced Quartus to put that in memory part of FPGA(Fig. 13).

```

1  `timescale 1ns/1ns
2
3  module ROM3(clk, address, dOut);
4      input clk;
5      input [7:0] address;
6      output reg [7:0] dOut;
7      (* ram_init_file = "sine.mif" *) reg [7:0] rom [255:0];
8      always @(posedge clk) begin
9          dOut = rom[address];
10     end
11 endmodule
12

```

Fig. 8 Memory Verilog description

```

1  `timescale 1ns/1ns
2
3  module ROM3(clk, address, dOut);
4      input clk;
5      input [7:0] address;
6      output reg [7:0] dOut;
7      (* ROMSTYLE = "M4K" *) (* ram_init_file = "sine.mif" *) reg [7:0] rom [255:0];
8      always @(posedge clk) begin
9          dOut = rom[address];
10     end
11 endmodule
12

```

Fig. 9 Memory Verilog description (ROMSTYLE is M4K)

Flow Summary	
Flow Status	Successful - Sun Apr 23 09:12:01 2023
Quartus II 32-bit Version	12.1 Build 177 11/07/2012 53 Web Edition
Revision Name	ROM3
Top-level Entity Name	ROM3
Family	Cyclone II
Device	EP2K10K10-10
Timing Models	Pin
Total logic elements	110 / 18,752 (< 1 %)
Total combinational functions	110 / 18,752 (< 1 %)
Dedicated logic registers	0 / 18,752 (0 %)
Total registers	0
Total pins	17 / 315 (5 %)
Total virtual pins	0
Total memory bits	0 / 239,616 (0 %)
Embedded Multiplier 9-bit elements	0 / 52 (0 %)
Total PLS	0 / 4 (0 %)

Fig. 10 Flow summary of syntheses of memory without memtoning ROMSTYLE: the total memory bits is zero which means that no memory block is used

 


Fig. 11 Chip planner: Blue blocks are LAB and dark blue blocks show used LAB



Flow Summary	
Flow Status:	Successful - Sun Apr 23 09:23:25 2023
Quartus II 32-bit Version:	12.1 Build 177 11/07/2012 S1 Web Edition
Revision Name:	ROM3
Top-level Entity Name:	ROM3
Family:	Cyclone II
Device:	EP2K10K10-10
Timing Models:	Fast
Total logic elements:	0 / 18,752 (0 %)
Total combinational functions:	0 / 18,752 (0 %)
Dedicated logic registers:	0 / 18,752 (0 %)
Total registers:	0
Total pins:	17 / 315 (5 %)
Total virtual pins:	0
Total memory bits:	2,048 / 239,616 (< 1 %)
Embedded Multiplier 9-bit elements:	0 / 52 (0 %)
Total PLLs:	0 / 4 (0 %)

Fig. 12 Flow summary of syntheses of memory with memtoring that ROMSTYLE is M4K: the total memory bits is 2048 which means that memory block is used. And the total logic element zero which mean no LAB is used.

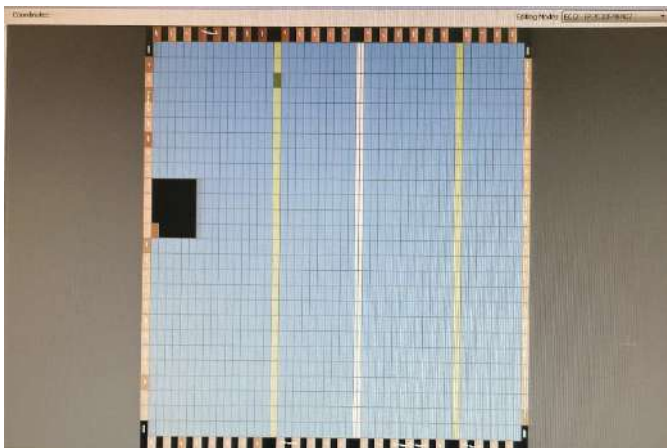


Fig. 13 Chip planner: green block show the used memory block  
For verifying the functionality of our design, we will test our design in Modelsim.

 


Fig. 14 waveform of signals

### III. DIGITAL TO ANALOG CONVERSION USING PWM

A) Verilog code for DAC module is shown in Fig. 15.

```

1  timescale 1ns/ 1ns
2
3  module PWM(clk, rst, data, PWM_out);
4      input clk, rst;
5      input [7:0] data;
6      output reg PWM_out;
7
8      reg [7:0] pulse_width = 8'b0;
9
10     always @(posedge clk) begin
11
12         if (rst) begin
13             pulse_width = 8'b0;
14         end
15
16         else begin
17
18             if (pulse_width == 8'b0) begin
19                 PWM_out = 1'b1;
20             end
21
22             if (pulse_width == data) begin
23                 PWM_out = 1'b0;
24             end
25
26             pulse_width = pulse_width + 1;
27         end
28     end
29 endmodule
30

```

Fig. 15 PWM Verilog code

B) The result of simulation of Modelsim is shown in Fig. 16.

 


Fig. 16 PWM waveform

C) After synthesising the design and programming FPGA, we connected output of the FPGA to oscilloscope and receive these waves by testing it.

 


Fig. 17 Reciprocal waveform

 


Fig. 18 Square waveform

 


Fig. 21 Full-wave rectified waveform



Fig. 19 Triangle waveform

 


Fig. 22 Half-wave rectified waveform

 


Fig. 20 Sine waveform

#### IV. FREQUENCY SELECTOR

In order to set the frequency of the output signal a frequency selector is required. The frequency selector consists of a counter that divides a high source input signal to the desired value. For this purpose, we will write a Verilog description of a simple 9 bit counter like Fig. 23.

 


Fig. 23 Block diagram of frequency selector

- 1) We will turn the 9 bit counter to frequency divider by wiring carry out signal to load enable signal.



```

1 timescale 1ns/1ns
2
3 module FrequencySelector(clk, rst, ld, parIn, clkOut):
4     input clk, rst, ld;
5     input [2:0] parIn;
6     output clkOut;
7     wire carryOut;
8     NineBitCounter counter(.clk(clk), .rst(rst), .ldEn(ld || carryOut),
9                             .parIn({parIn, 6'b0}), .cOut(carryOut));
10    assign clkOut = carryOut;
11 endmodule
12

```

Fig. 24 frequency selector Verilog code

- 2) for testing the design, we show the sine wave in four different frequencies.

Each period of sine wave will be completed by 400 clock cycles.

So the frequency of sine wave can be calculated by following formula:

$$f_{sine} = \frac{f_{clk}}{400 \times (512 - PI - 1)}$$

Where PI is parallel input of frequency selector.

$$PI = 256_d$$

$$f_{sine} = \frac{50 \text{ MHz}}{400 \times (512 - 256 - 1)} = 490.19 \text{ Hz}$$

 


Fig. 27 Sine wave ( $PI = 1_0100_0000_b$ )

$$PI = 320_d$$

$$f_{sine} = \frac{50 \text{ MHz}}{400 \times (512 - 320 - 1)} = 654.45 \text{ Hz}$$

 


Fig. 25 Sine wave ( $PI = 0_0000_0000_b$ )

$$PI = 0_d$$

$$f_{sine} = \frac{50 \text{ MHz}}{400 \times (512 - 0 - 1)} = 244.61 \text{ Hz}$$

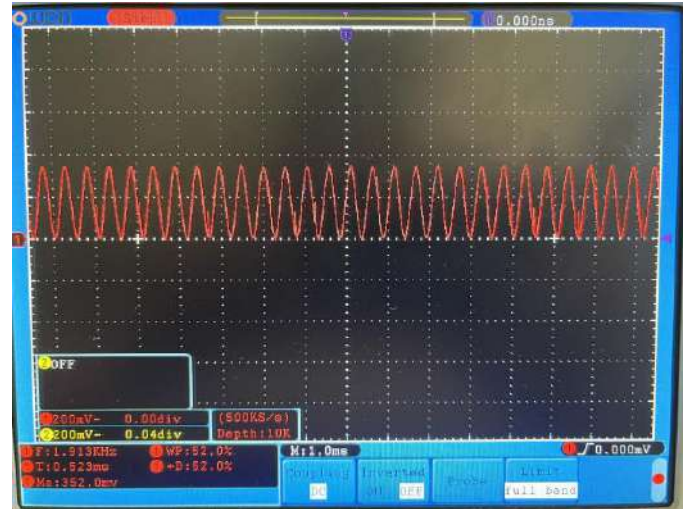


Fig. 28 Sine wave ( $PI = 1_1100_0000_b$ )

$$PI = 448_d$$

$$f_{sine} = \frac{50 \text{ MHz}}{400 \times (512 - 448 - 1)} = 1.98 \text{ KHz}$$

Calculated frequencies are approximately equal to observed ones.

## V. AMPLITUDE SELECTOR

 


Fig. 26 Sine wave ( $PI = 1_0000_0000_b$ )

One option in function generator is the amplitude of generated wave. The task of this module is to scale down the amplitude of the waveforms. This can be done by dividing the output amplitude by a number. The value of divisor is chosen by a 2-bit input. Dedicate two bits of input SW (SW[6:5]) to this selector inputs. This module divides the amplitude of the output wave by the numbers of following table.

Table 1: Amplitude selection

SW[6:5]	Amplitude
2'b00	1
2'b01	2
2'b10	4
2'b11	8

 


Fig. 29 Square wave (Amplitude: 1)

$$Domain = 360\text{ mV}$$



Fig. 30 Square wave (Amplitude: 2)

$$Domain = \frac{360}{2} = 180\text{ mV}$$



Fig. 31 Square wave (Amplitude: 4)

$$Domain = \frac{360}{4} = 90\text{ mV}$$





Fig. 32 Square wave (Amplitude: 8)

$$Domain = \frac{360}{8} = 40 \text{ mV}$$

## VI. THE TOTAL DESIGN

The final block diagram is shown if Fig. 33.

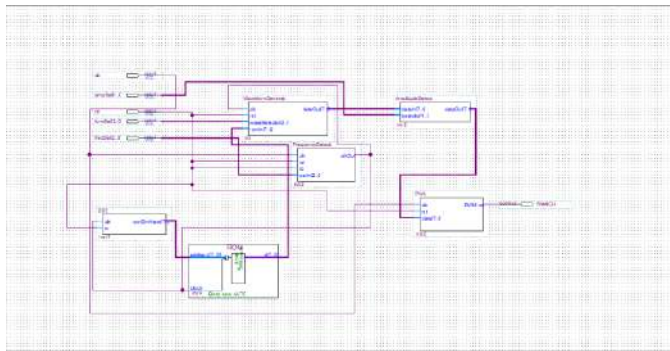


Fig. 33 Final block diagram in Quartus II

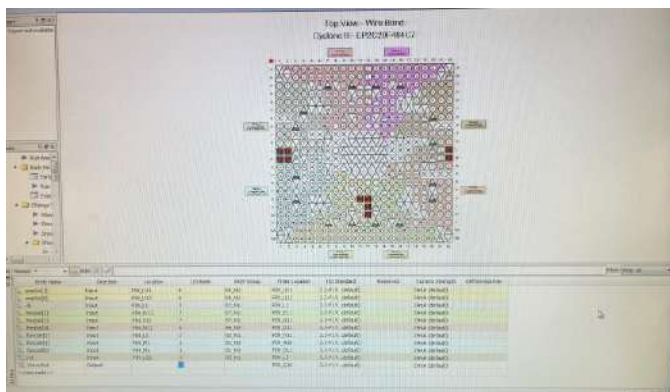


Fig. 34 Pin planner

## VII. CONCLUSIONS

By designing the components of the waveform generator, frequency selector, amplitude selector, and DAC modules in Verilog, and synthesizing the project in Quartus II, we

programmed the FPGA. The project successfully achieved its objectives of generating various waveforms with adjustable frequency and amplitude, and the final design was able to integrate all the modules seamlessly. We tested and verified the functionality of the design through the use of oscilloscope.

## ACKNOWLEDGMENT

This report was prepared and developed by Mehdi Jamalkhah and Mobina Mehrazar, bachelor students of Computer engineering at University of Tehran, under the supervision of professor Zain Navabi.